LAB – 1

INVERTER

K.N Sujay 121910402035

Outputs:

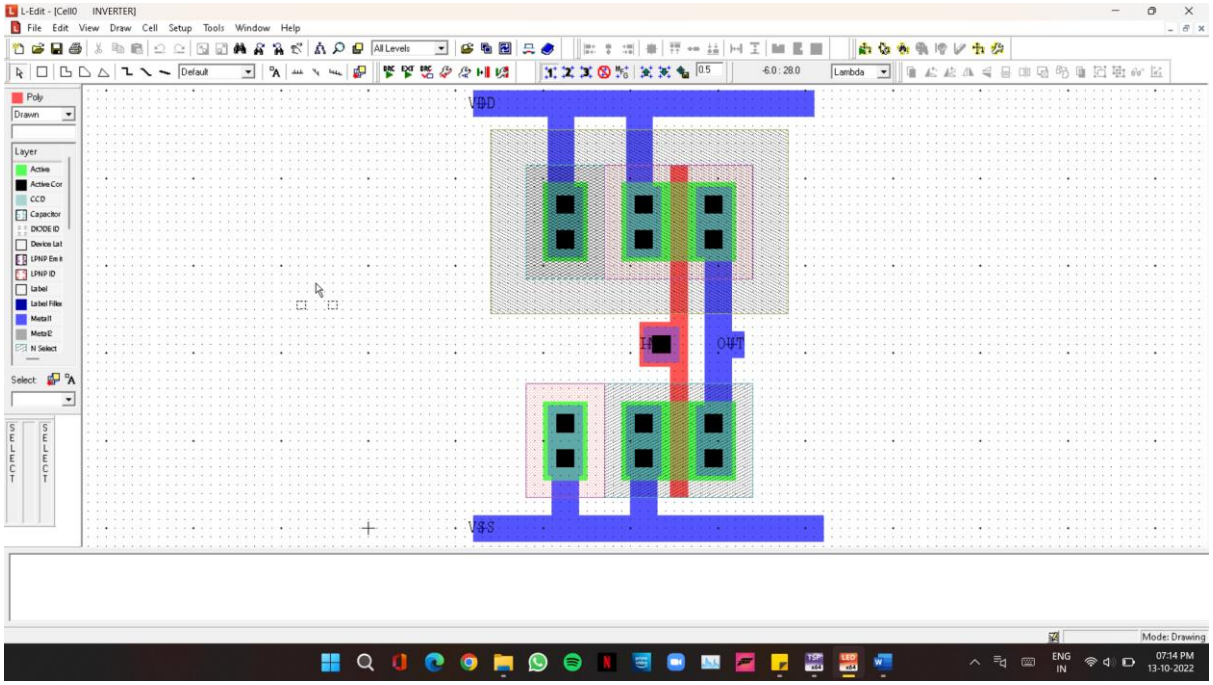

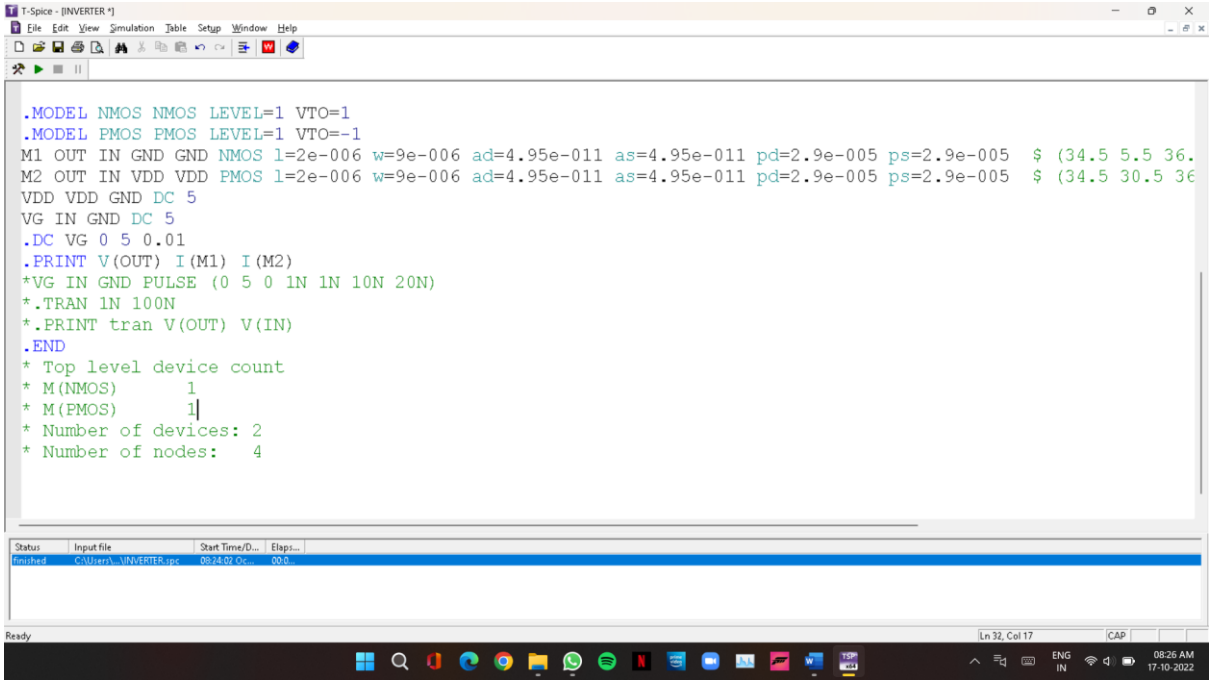

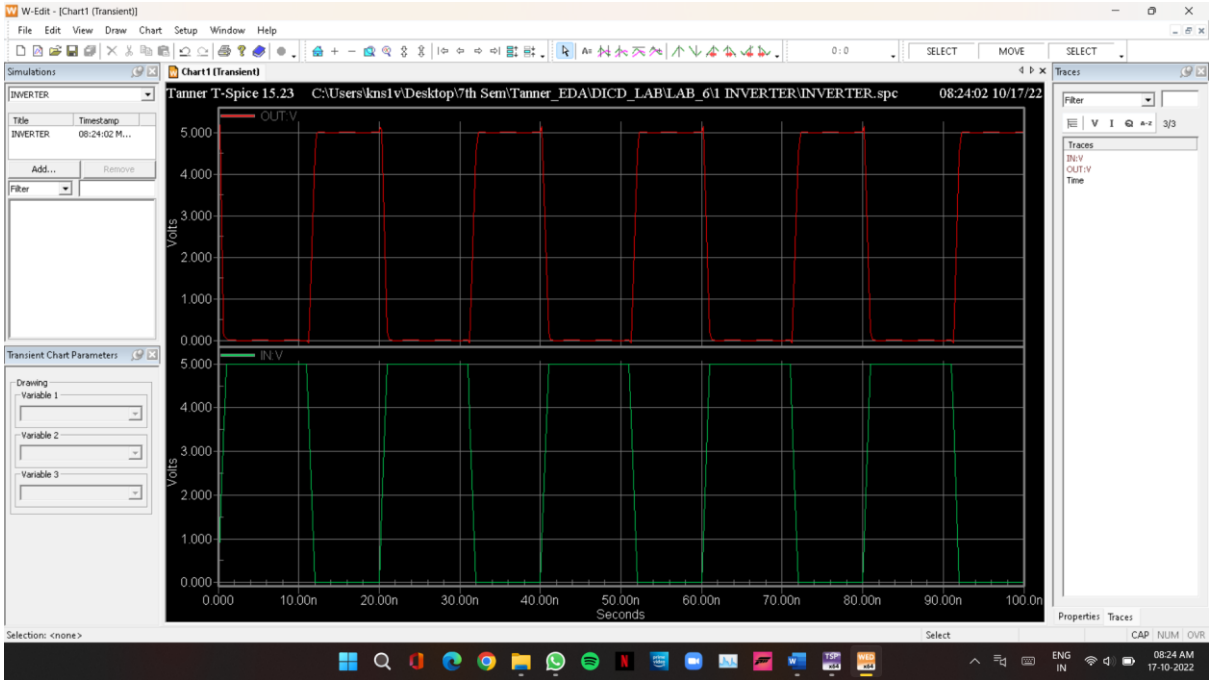
W-Edit - [Chart1 (Transient)]
Chart1 (Transient)
Tanner T-Spice 15.23 C:\Users\kns1v\Desktop\7th Sem\Tanner_EDA\DICD_LAB\LAB_6\1 INVERTER\INVERTER.spc 08:24:02 10/17/22
OUT:V
IN:V
Volts
Seconds
0.000
10.00n
20.00n
30.00n
40.00n
50.00n
60.00n
70.00n
80.00n
90.00n
100.0n

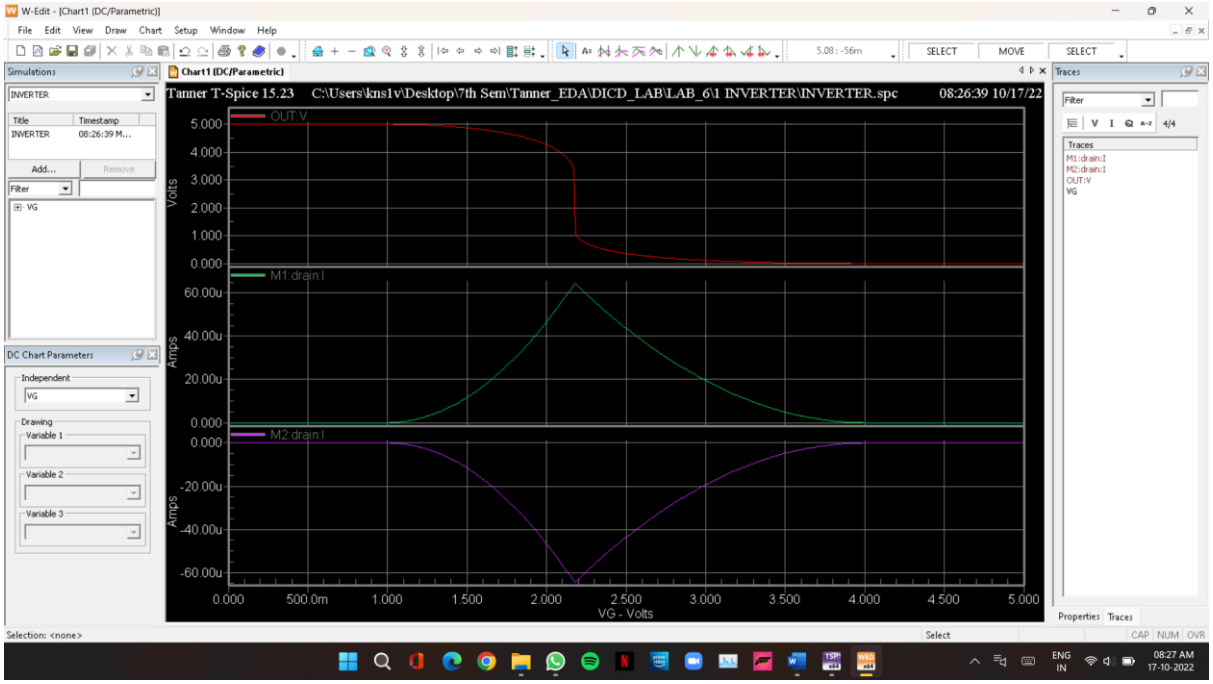
W-Edit - [Chart1 (DC/Parametric)]
Chart1 (DC/Parametric)
Tanner T-Spice 15.23 C:\Users\kns1v\Desktop\7th Sem\Tanner_EDA\DICD_LAB\LAB_6\1 INVERTER\INVERTER.spc 08:26:39 10/17/22
OUT:V
M1:drain:I
M2:drain:I
Volts
Amps
VG - Volts
0.000
500.0m
1.000
1.500
2.000
2.500
3.000
3.500
4.000
4.500
5.000